
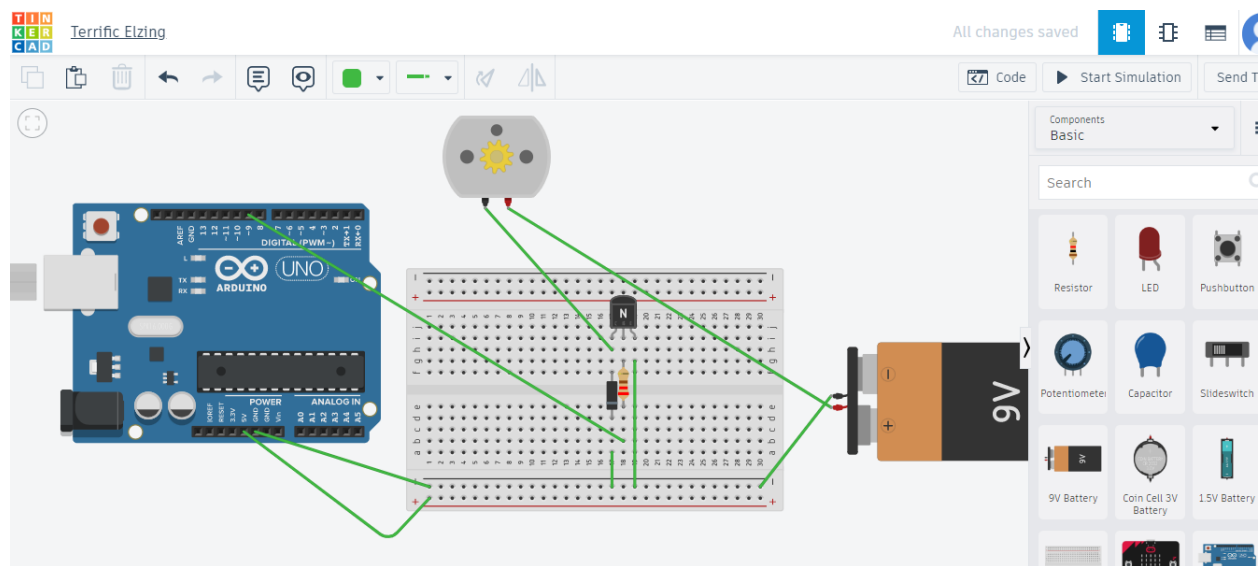


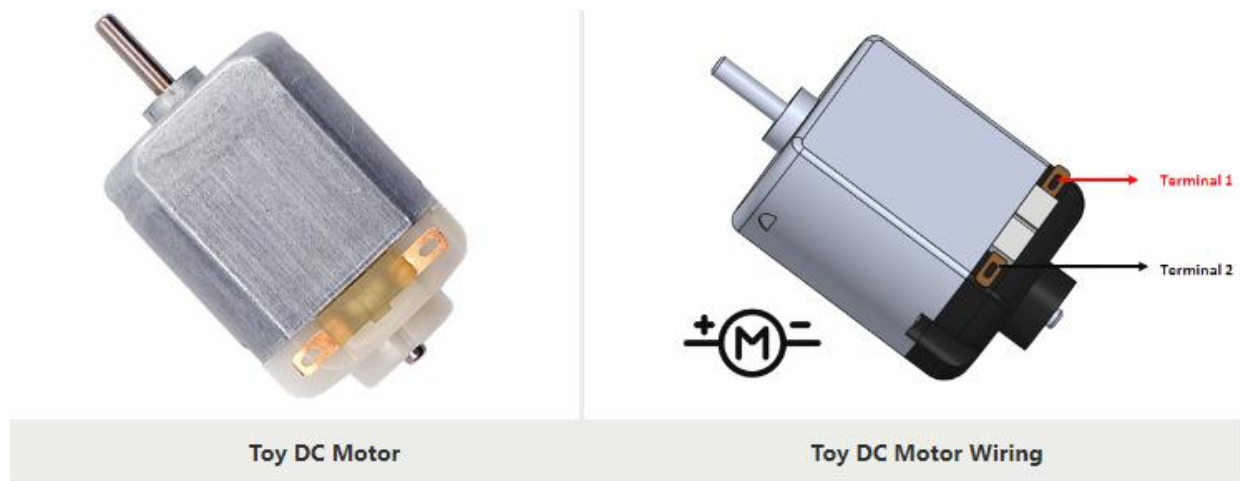Program to demonstrate DC motor using Arduino uno in tinkercad step by step in a simple and easy way



Step 1: Set Up Tinkercad

1. **Log in** to Tinkercad.
2. Click on “**Circuits**” and then “**Create new Circuit.**”

Step 2: Add Components

1. **Arduino Uno**: Drag it onto the workspace.
2. **DC Motor**: Add it to the workspace.

3. **9V Battery**: Drag it into the circuit.
4. **NPN Transistor** (e.g., 2N2222): Add it.
5. **Diode** (e.g., 1N4007): Add it.
6. **Resistor** (220Ω): Place it in the workspace.
7. (Optional) **Breadboard**: Add it for organization.

Step 3: Wire the Components

1. **Motor**:
 - Connect one terminal to the **collector** of the NPN transistor.
 - Connect the other terminal to the **positive** terminal of the battery.
2. **Diode**:
 - Connect the **anode** (no stripe) to the collector.
 - Connect the **cathode** (stripe) to the **negative** terminal of the battery.
3. **Transistor**:
 - Connect the **emitter** to the **ground (GND)** rail.
 - Connect the **base** to one end of the resistor; connect the other end to **digital pin 9** on the Arduino.
4. **Power Connections**:
 - Connect the **negative terminal** of the battery to the GND rail.
 - Connect the **GND** pin of the Arduino to the GND rail.

Step 4: Write the Arduino Code

1. Click the “**Code**” button.
2. Replace the default code with:

```
int motorPin = 9; // Motor control pin

void setup() {
  pinMode(motorPin, OUTPUT); // Set pin as output
}

void loop() {
  digitalWrite(motorPin, HIGH); // Turn motor ON
  delay(2000);                  // Wait for 2 seconds
  digitalWrite(motorPin, LOW);  // Turn motor OFF
  delay(2000);                  // Wait for 2 seconds
}
```

Step 5: Simulate the Circuit

1. Click **“Start Simulation.”**
2. Observe the motor: it should turn on for 2 seconds and then off for 2 seconds, repeating this cycle.

Step 6: Debugging (if needed)


- **Check connections:** Ensure they are correct.
- **Verify code:** Ensure there are no syntax errors.

Conclusion

You've successfully set up a DC motor controlled by an Arduino Uno! The motor will turn on and off in a loop as programmed. Enjoy experimenting!

An **NPN transistor** is a device that can control a larger electrical current using a smaller one.

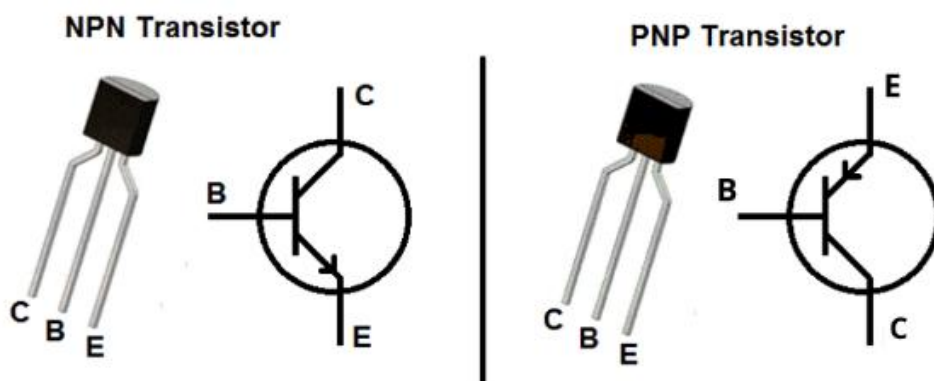
You can think of an NPN transistor like a water faucet. When you turn the handle (the base), it allows a larger flow of water (current) to come out from the pipe (collector) to the drain (emitter). A little twist controls a much bigger flow! a small turn (input current) controls a larger flow of water (output current) from the pipe.



– base terminal; E – emitter terminal; C – collector terminal

- A **diode** is a semiconductor device that allows current to flow in one direction only, acting as a one-way valve for electrical current. It consists of a p-n junction and is used in various

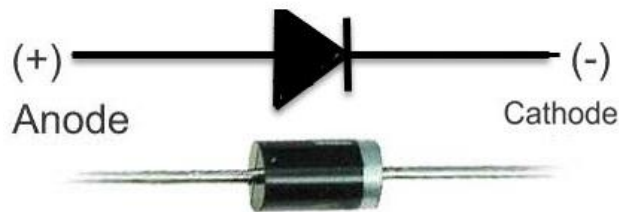applications like rectification, voltage regulation, and signal demodulation. In circuits, diodes protect components from reverse polarity and voltage spikes.



1N4007 Diode Pinout



1N4007 Diode Electronic Symbol



```
int motorPin = 9; // Motor control pin
```

```
void setup() {
```

```
  pinMode(motorPin, OUTPUT); // Set pin as output
```

```
}
```

```
void loop() {
```


```
    digitalWrite(motorPin, HIGH); // Turn motor ON
```

```
    delay(2000);                // Wait for 2 seconds
```

```
    digitalWrite(motorPin, LOW); // Turn motor OFF
```

```
    delay(2000);                // Wait for 2 seconds
```

```
}
```

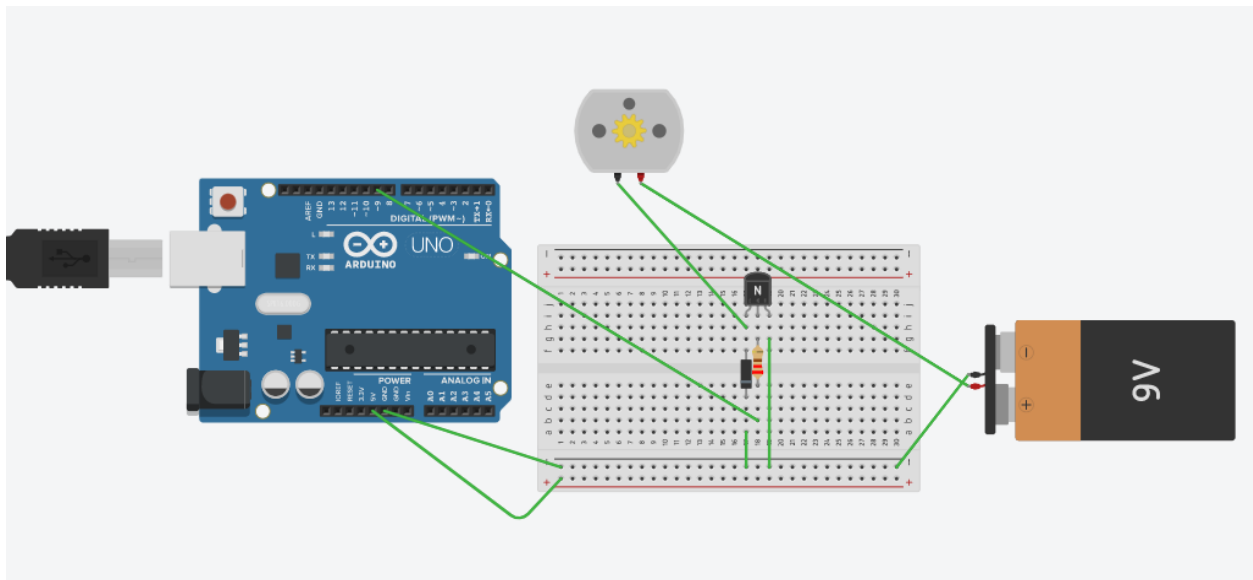

```
int motorPin = 9; // Motor control pin
```

```
void setup() {
```

```
pinMode(motorPin, OUTPUT); // Set pin as output  
}
```

```
void loop() {  
  digitalWrite(motorPin, HIGH); // Turn motor ON  
  delay(2000);                // Wait for 2 seconds  
  digitalWrite(motorPin, LOW); // Turn motor OFF  
  delay(2000);                // Wait for 2 seconds  
}
```